

# **COMP2611: Computer Organization**

## **Arithmetic for Computers**

- ❑ Revisit addition & subtraction for **2's complement** numbers
- ❑ Explain the construction of a 32-bit **arithmetic logic unit (ALU)**
- ❑ Show algorithms and implementations of **multiplication** and **division**
- ❑ Demonstrate **floating-point** arithmetic operations

# 1. 2's Complement Arithmetic

- ❑ **Bits**: the basis for **binary number representation** in digital computers
  
- ❑ We've learnt:
  - ✓ How to represent **negative numbers**
  - ✓ How to represent **fractions** and **real numbers**
  - ✓ What is the **representable range**

## ❑ Signed numbers

- **negative** or **non-negative** integers, e.g. `int` in C/C++

## ❑ Unsigned numbers

- **non-negative** integers, e.g. `unsigned int` in C/C++

## ❑ Operations for unsigned numbers

- Comparison:

`sltu` (set on less than unsigned), `sltiu`

- Arithmetic:

`addu`, `subu` (add/subtract unsigned)

- Treat values of all registers as non-negative

`addiu` (add unsigned sign-extended immediate)

- The 16-bit immediate is sign-extended then addition as above

`addi` (add signed immediate)

- Load:

`lbu` (load byte unsigned), `lhu` (load half unsigned)

- ❑  $\$s0$  1111 1111 1111 1111 1111 1111 1111 1111<sub>2</sub>
- ❑  $\$s1$  0000 0000 0000 0000 0000 0000 0000 0001<sub>2</sub>
  
- ❑ What are the values in registers  $\$t0$  and  $\$t1$  in the examples below?
  - `slt $t0, $s0, $s1` # signed comparison  
 $\$s0 = -1_{10}$ ,  $\$s1 = 1_{10}$ ,  $\$t0 = 1$
  - `sltu $t1, $s0, $s1` # unsigned comparison  
 $\$s0 = 4294967295_{10}$ ,  $\$s1 = 1_{10}$ ,  $\$t1 = 0$

- ❑ Operands in instruction may have mis-matched sizes

`addi $t0, $s0, -5` # add 32-bit operands in \$s0 with 16-bit immediate value in 2's complement

`ori $t0, $s0, 0xFB32`

`lb $t0, 0($s0)` # load a 8-bit signed number to 32-bit register

- ❑ Need conversion from **n**-bit binary numbers into **m**-bit numbers (**m** > **n**)

- ❑ **Sign extension:** Fill the leftmost bits (**n**-th ~ (**m**-1)-th) with the sign bit

2 (16 bits -> 32 bits):

0000 0000 0000 0010 -> 0000 0000 0000 0000 0000 0000 0000 0010

-2 (16 bits -> 32 bits):

1111 1111 1111 1110 -> 1111 1111 1111 1111 1111 1111 1111 1110

`addi, lb`

- ❑ **Zero extension:** Pad the leftmost bits (**n**-th ~ (**m**-1)-th) with 0

- ❑ `and, or`

- ❑ add immediate unsigned `addiu $t0, $s1, 0xFB32`
- ❑ Zero extended? **WRONG**
  
- ❑ MIPS unsigned arithmetic operations: `addu`, `addiu`, `subu`, `subiu`, `sltu`, `sltiu`
  
- ❑ The immediate fields of `addiu`, `sltiu` are **sign-extended!**

The MIPS32 Instruction Set states that the word 'unsigned' as part of add and subtract instructions, is a misnomer. The difference between signed and unsigned versions of commands is not a sign extension of the operands, but controls whether a trap is executed on overflow (i.e. `add`) or an overflow is ignored (i.e. `addu`). An immediate operand `CONST` to these instructions is always sign-extended.



## ❑ Addition

Bits are added bit by bit **from right to left**, with **carries** passed to the next bit position to the left

## ❑ Subtraction

### **Subtraction uses addition**

The appropriate operand is **negated** before being added to the other operand

## ❑ Overflow

The result is too large to fit into a word (32 bits in MIPS)



□ **Addition** ( $1073741824 + 1073741824 = 2147483648$ ):

$$\begin{array}{r}
 0100\ 0000\ 0000\ 0000\ 0000\ 0000\ 0000\ 0000_2 = 1073741824_{10} \\
 + 0100\ 0000\ 0000\ 0000\ 0000\ 0000\ 0000\ 0000_2 = 1073741824_{10} \\
 \hline
 = 1000\ 0000\ 0000\ 0000\ 0000\ 0000\ 0000\ 0000_2 \neq 2147483648_{10}
 \end{array}$$

In 2's complement the MSb is a sign bit  
then, it means  $-2147483648_{10}$

## Addition ( $X + Y$ )

- ❑ No overflow occurs when:  
X and Y are of different signs
- ❑ Overflow occurs when:  
X and Y are of the same sign  
But,  $X + Y$  is represented in a different sign

## ❑ Overflow condition

Operation	Sign Bit of X	Sign Bit of Y	Sign Bit of Result
$X + Y$	0	0	1
$X + Y$	1	1	0
$X - Y$	0	1	1
$X - Y$	1	0	0

## Subtraction ( $X - Y$ )

- ❑ No overflow occurs when:  
X and Y are of the same sign
- ❑ Overflow occurs when:  
X and Y are of different signs  
But,  $X - Y$  is represented in a different sign from X

MIPS detects overflow with an **exception** (also called an **interrupt**)

- ❑ Exceptions occur when unscheduled events disrupt program execution
- ❑ Some instructions are designed to cause exceptions on overflow
  - e.g. **add**, **addi** and **sub** cause exceptions on overflow
  - But, **addu**, **addiu** and **subu** do **not** cause exceptions on overflow;
  - programmers are responsible for using them correctly**

When an overflow exception occurs

- ❑ Control jumps to a **predefined address (code)** to **handle the exception**
- ❑ The interrupted address is saved to **EPC** for possible resumption
  - EPC = exception program counter**; a special register
  - MIPS software return to the offending instruction via jump register


## 2. Arithmetic Logic Unit

- ❑ The **arithmetic logic unit (ALU)** of a computer is the hardware component that performs:


**Arithmetic operations** (like addition and subtraction)

**Logical operations** (like AND and OR)

## Processor

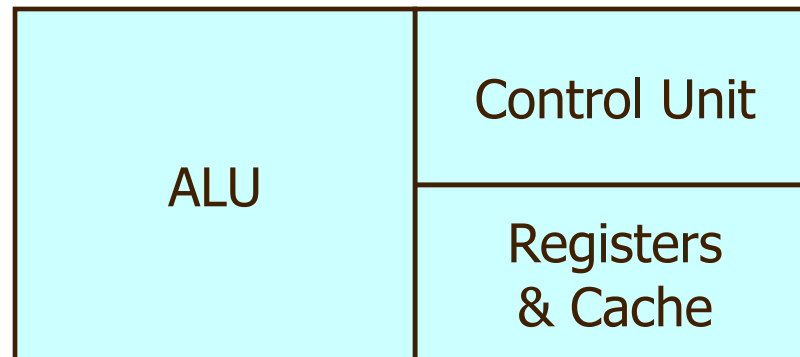


 
- ❑ Since a word in MIPS is 32 bits wide, we need a 32-bit ALU
- ❑ Ideally, we can build a 32-bit ALU by connecting 32 1-bit ALUs together (each of them takes care of the operation on one bit position)
- ❑ **1-bit** logical unit for AND and OR:



A multiplexor selects the appropriate result depending on the operation specified



  - ❑ An adder must have
  - Two inputs (bits) for the **operands**
  - A single-bit output for the **sum**
- ❑ Also, must have a second output to pass on the carry, called **carry-out**
  - Carry-out becomes the **carry-in** to the neighbouring adder
- ❑ 1-bit full adder is also called a **(3, 2) adder** (3 inputs and 2 outputs)



□ Truth table:


Inputs			Outputs		Comments
a	b	CarryIn	CarryOut	SumOut	
0	0	0	0	0	$0 + 0 + 0 = 00_2$
0	0	1	0	1	$0 + 0 + 1 = 01_2$
0	1	0	0	1	$0 + 1 + 0 = 01_2$
0	1	1	1	0	$0 + 1 + 1 = 10_2$
1	0	0	0	1	$1 + 0 + 0 = 01_2$
1	0	1	1	0	$1 + 0 + 1 = 10_2$
1	1	0	1	0	$1 + 1 + 0 = 10_2$
1	1	1	1	1	$1 + 1 + 1 = 11_2$

□ Logic equations:

$$\begin{aligned} \text{CarryOut} &= (b \times \text{CarryIn}) + (a \times \text{CarryIn}) + (a \times b) + (a \times b \times \text{CarryIn}) \\ &= (b \times \text{CarryIn}) + (a \times \text{CarryIn}) + (a \times b) \end{aligned}$$

$$\begin{aligned} \text{SumOut} &= (a \times \overline{b} \times \overline{\text{CarryIn}}) + (\overline{a} \times b \times \overline{\text{CarryIn}}) + (\overline{a} \times \overline{b} \times \text{CarryIn}) \\ &\quad + (a \times b \times \text{CarryIn}) \end{aligned}$$
 
$$\begin{aligned}\square \text{ CarryOut} &= (b \cdot \text{CarryIn}) + (a \cdot \text{CarryIn}) + (a \cdot b) + (a \cdot b \cdot \text{CarryIn}) \\ &= (b \cdot \text{CarryIn}) + (a \cdot \text{CarryIn}) + (a \cdot b)\end{aligned}$$



$\square$  SumOut bit: (It is left as an exercise)


## □ 3 in 1 building block

Use the **Operation** bits to decide what result to push out

Operation = 0, do **AND**

Operation = 1, do **OR**


Operation = 2, do **addition**

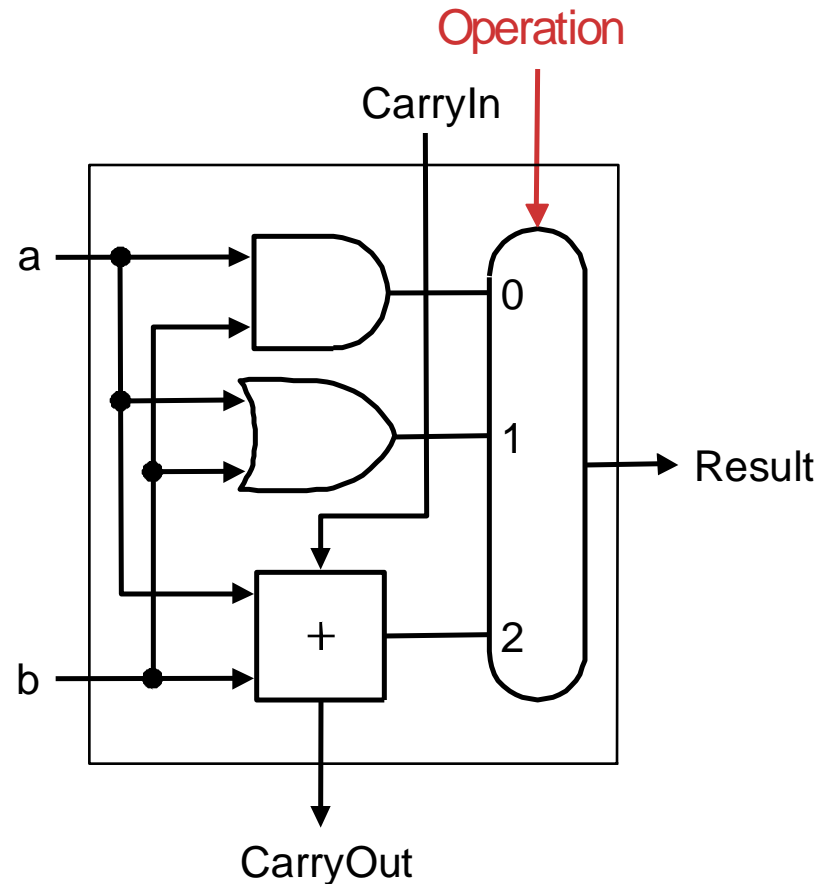

- ❑ **Ripple carry** organization of a 32-bit ALU constructed from 32 1-bit ALUs:


A single carry out of the least significant bit (**Result0**) could ripple all the way through the adders, causing a carry out of the most significant bit (**Result31**)

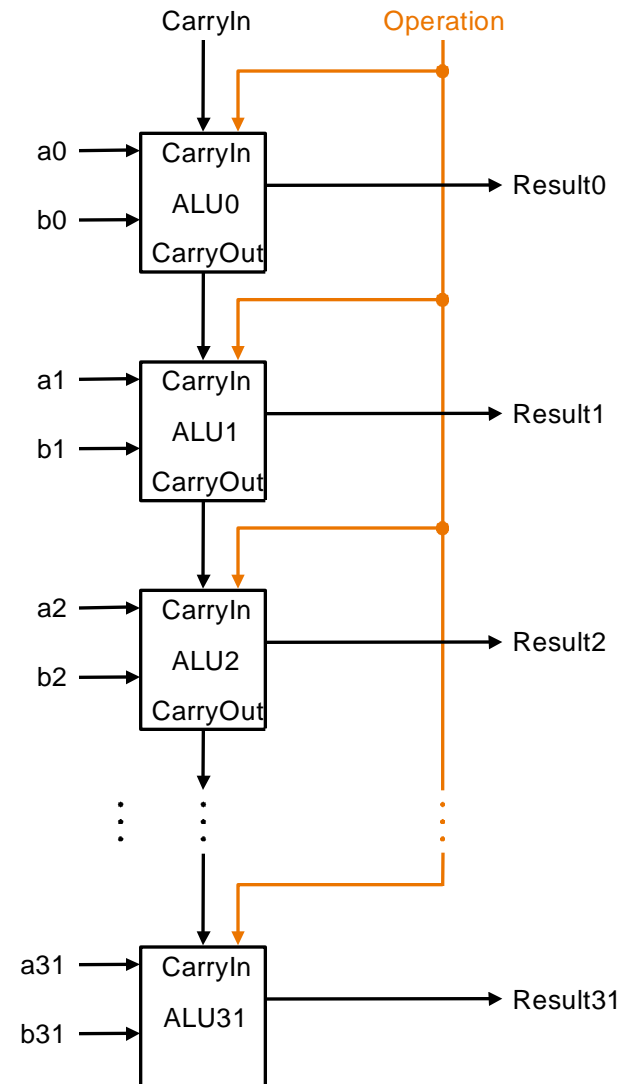There exist more efficient implementations (based on the **carry lookahead** idea to be explained later)



- ❑ **Subtraction** is the same as adding the negated operand
- ❑ By doing so, an adder can be used for both addition and subtraction
- ❑ A 2:1 **multiplexor** is used to choose between
  - an operand (for **addition**) and
  - its negative version (for **subtraction**)
  
- ❑ **Shortcut** for negating a 2's complement number:
  - Invert each bit (to get the 1's complement representation)
  - Add 1: Obtained by setting the ALU0's carry bit to 1

 - ❑ To execute  $a - b$  we can execute  $a + (-b)$
- ❑ **Binvert**: the selector input of a multiplexor to choose between addition and subtraction



- ❑ To form a 32-bit ALU, connect 32 of these 1-bit ALUs
- ❑ To negate  $b$  we must invert it and add 1 (2's complement), so we must Set CarryIn input of the least significant bit (ALU0) to 1 for subtraction

- ❑ The 32-bit ALU being designed so far can perform **add, sub, and, or** operations which constitute a large portion of MIPS' instruction set
- ❑ Two instructions not yet supported are: **slt** and **beq**
  
- ❑ When we need to compare **Rs** to **Rt**
  - By definition of **slt**, if **Rs < Rt**
    - LSb of the output is set to **1**
    - Otherwise, it is reset to **0**
- ❑ How to implement it?
  - The comparison is equivalent to testing if **(Rs - Rt) < 0**
  - If **(Rs - Rt)** is smaller than **0**
    - MSb of the subtraction **(Rs - Rt)** equals to **1** (means negative)
    - Otherwise, MSb of the subtraction equals to **0**
  - Notice that the outcome of MSb is similar to the result of **slt**
  - ☑ Idea: **copy the MSb of the subtraction result to the LSb of slt's output. All other bits of the output are 0**
  - ☑ **slt** can be done using two types of 1-bit ALUs




□ How to implement it?


○ The comparison is equivalent to testing if  $(R_s - R_t) < 0$

```
slt $t0, $s1, $s2
```


If  $R_s - R_t \geq 0$

 


If  $R_s - R_t < 0$

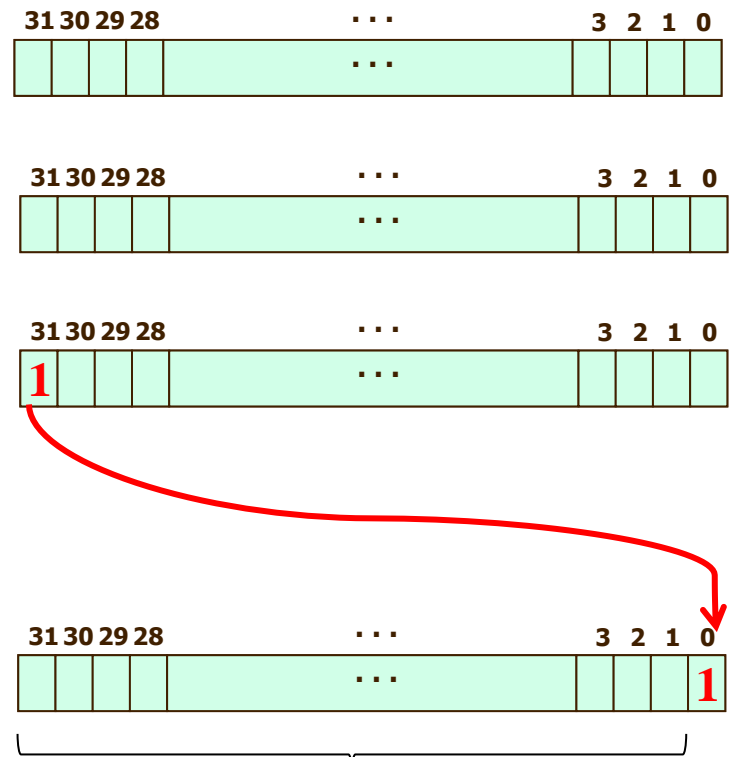

All 0

 


1-bit ALU for bits 0 to 30

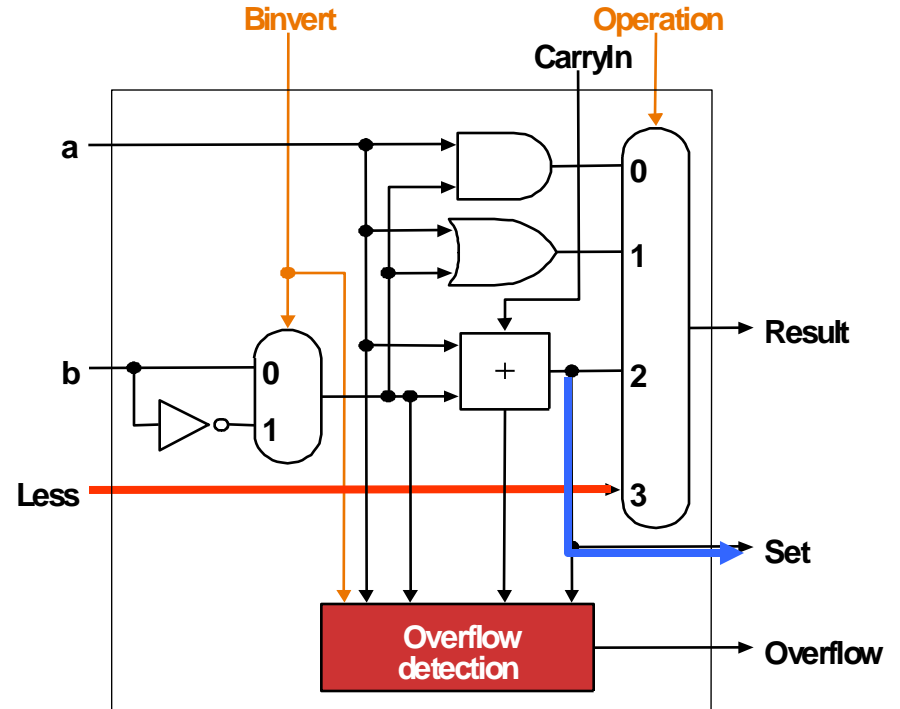


1-bit ALU for the MSb (bit 31)

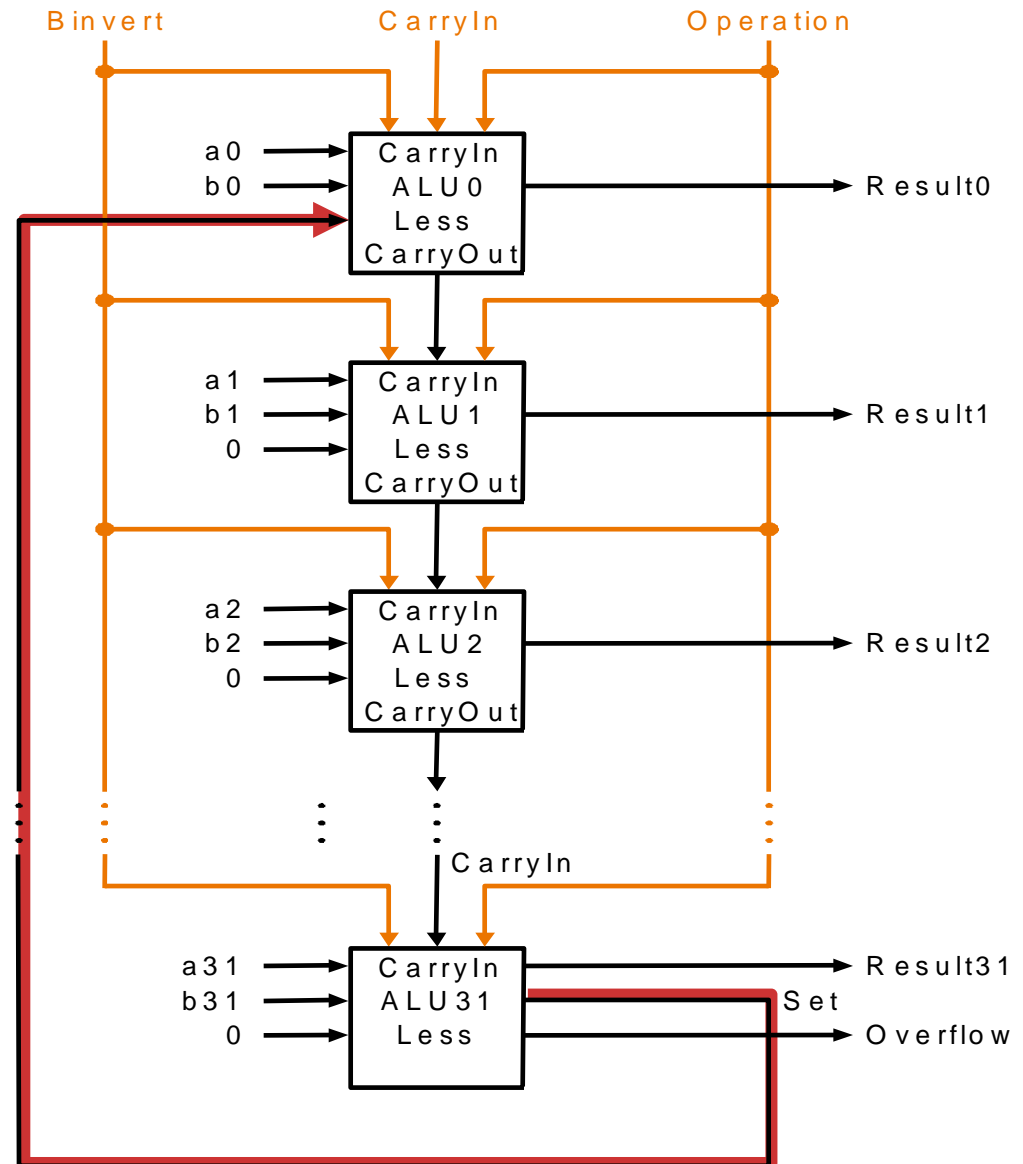- ❑ The “set” signal is the MSb of the result of the subtraction,  $A - B$
- ❑ It is passed to LSB
- ❑ Result0 will equal to this “set” signal when operation = 3 (which means `slt` instruction is being executed)




- ❑ To support `beq`
  
- ❑ We need to compare `Rs` to `Rt`
  - The comparison is equivalent to testing if  $(Rs - Rt) == 0$
  - If  $(Rs - Rt)$  is equal to 0
    - All bits of the output are 0
    - Otherwise, at least one of them is non 0

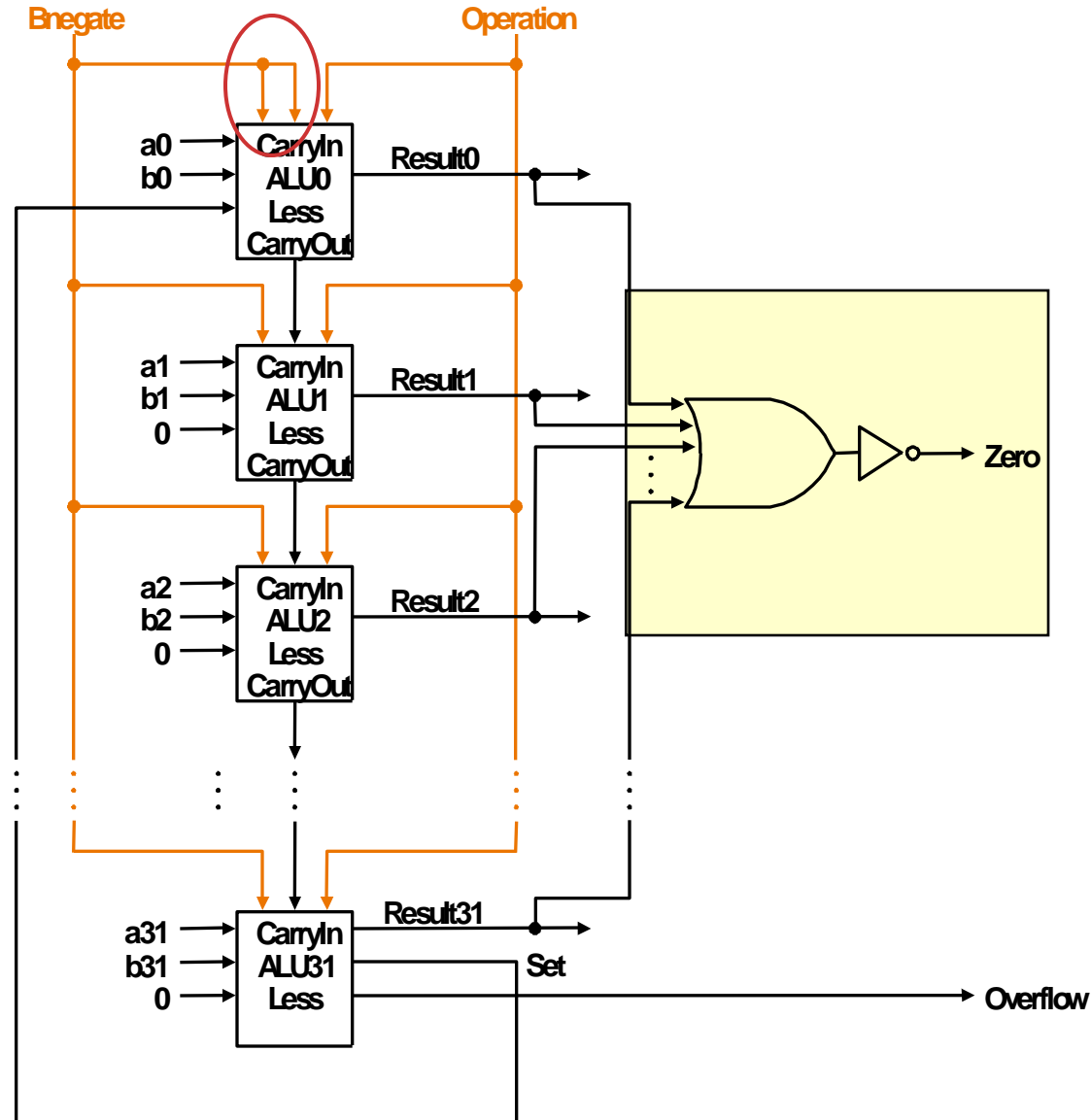- ❑ Finally, this adds a zero detector
- ❑ For addition and AND/OR operations both **Bnegate** and **CarryIn** are 0 and for subtract, they are both 1 so we combine them into a single line



 - Knowing what is exactly inside a 32-bits ALU, from now on we will use the universal symbol for a complete ALU as follows:



ALU Control lines	Operation
000	AND
001	OR
010	ADD
110	SUB
111	SLT

- ❑ Using the ripple carry adder, the carry has to propagate from the LSB to the MSb in a sequential manner, passing through all the 32 1-bit adders one at a time. **SLOW** for time-critical hardware!
- ❑ Key idea behind fast carry schemes **without the ripple effect**:

$$\text{CarryIn}_2 = (b_1 \cdot \text{CarryIn}_1) + (a_1 \cdot \text{CarryIn}_1) + (a_1 \cdot b_1)$$

$$\text{CarryIn}_1 = (b_0 \cdot \text{CarryIn}_0) + (a_0 \cdot \text{CarryIn}_0) + (a_0 \cdot b_0)$$

Substituting the latter into the former, we have:

$$\begin{aligned} \text{CarryIn}_2 = & (a_1 \cdot a_0 \cdot b_0) + (a_1 \cdot a_0 \cdot \text{CarryIn}_0) + (a_1 \cdot b_0 \cdot \text{CarryIn}_0) \\ & + (b_1 \cdot a_0 \cdot b_0) + (b_1 \cdot a_0 \cdot \text{CarryIn}_0) + (b_1 \cdot b_0 \cdot \text{CarryIn}_0) \\ & + (a_1 \cdot b_1) \end{aligned}$$

All other CarryIn bits can also be expressed using CarryIn<sub>0</sub>

- ❑ A Bit position generates a Carry iff both inputs are 1:  $G_i = a_i \cdot b_i$
- ❑ A Bit position propagates a Carry if exactly one input is 1:  $P_i = a_i + b_i$
- ❑ Carryout at bit  $i$  can be expressed as:

$$C_i = G_i + P_i \cdot C_{i-1}$$


- ❑ After substitution we have

$$C_1 = G_0 + P_0 C_0$$

$$C_2 = G_1 + G_0 P_1 + C_0 P_0 P_1$$

$$C_3 = G_2 + G_1 P_2 + G_0 P_1 P_2 + C_0 P_0 P_1 P_2$$
 
$$C_4 = G_3 + G_2 P_3 + G_1 P_2 P_3 + G_0 P_1 P_2 P_3 + C_0 P_0 P_1 P_2 P_3$$



- ❑ WE can build a circuit to predict all Carries at the same time and do the additions in parallel
- ❑ Possible because electronic chips becoming cheaper and denser



